

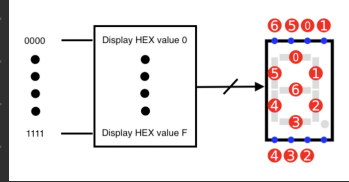


1. In your lab report, derive seven truth tables, one for each segment of the 7-segment decoder.
Another way to ask this question is: which segments should be on (and which should be off) for a given character?

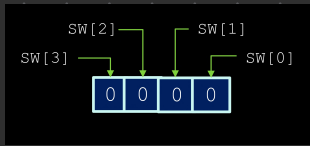

Segment 0

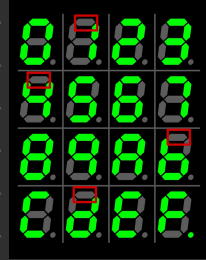- ON at all times BUT
→ 1, 4, 6, d
→ 0001, 0100, 1011, 1101



D _{3:0}	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	E
1111	F



All combinations of SW1, SW0

All combinations of SW3, SW2


	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * SW0$ 1 1	$SW1 * \overline{SW0}$ 1 0
$\overline{SW3} * \overline{SW2}$ 0 0	1	0	1	1
$\overline{SW3} * SW2$ 0 1	0	1	1	1
$SW3 * \overline{SW2}$ 1 1	1	0	1	1
$SW3 * SW2$ 1 0	1	1	0	1

$$\begin{aligned}
 &\overline{SW2} \cdot \overline{SW0} \\
 &\overline{SW3} \cdot SW1 \\
 &SW2 \cdot SW1 \\
 &SW3 \cdot SW0 \\
 &\overline{SW3} \cdot SW2 \cdot SW0 \\
 &SW3 \cdot \overline{SW2} \cdot \overline{SW1}
 \end{aligned}$$

		will be 0 when	SW3	SW2	SW1	SW0
+	A 3		0	0	0	1
+	B 2		0	1	0	0
+	C 1		1	0	1	1
+	D 0		1	1	0	1

Segment 1

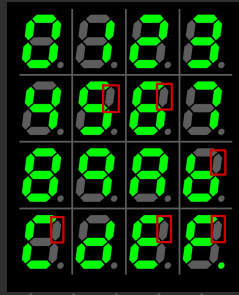- ON at all times but
→ 0101, 0110, 1011, 1100, 1110, 1111
5, 6, b, c, E, F



D ₃₀	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	a
1011	b
1100	c
1101	d
1110	e
1111	f



	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * \overline{SW0}$ 1 0	$SW1 * SW0$ 1 1
$\overline{SW3} * \overline{SW2}$ 0 0	1	1	1	1
$\overline{SW3} * SW2$ 0 1	1	0	1	0
$SW3 * \overline{SW2}$ 1 0	0	1	0	0
$SW3 * SW2$ 1 1	1	1	0	1


$\overline{SW3} \cdot \overline{SW2} +$
 $\overline{SW0} \cdot \overline{SW2} +$
 $\overline{SW0} \cdot \overline{SW1} \cdot \overline{SW3} +$
 $\overline{SW3} \cdot \overline{SW1} \cdot \overline{SW0} +$
 $SW3 \cdot \overline{SW1} \cdot SW0$

A 3
 B 2
 C 1
 D 0

Will be 0 when:

SW3	SW2	SW1	SW0
0	1	0	1
0	1	1	0
1	0	1	1
1	1	0	0
1	1	1	0
1	1	1	1

Segment 2

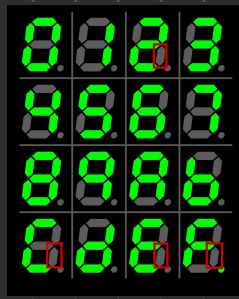

D _{3:0}	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	e
1111	f



	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * \overline{SW0}$ 1 1	$SW1 * SW0$ 1 0
$\overline{SW3} * \overline{SW2}$ 0 0	1	1	1	0
$\overline{SW3} * SW2$ 0 1	1	1	1	1
$SW3 * \overline{SW2}$ 1 1	0	1	0	0
$SW3 * SW2$ 1 0	1	1	1	1


$$\begin{aligned}
 &\overline{SW3} \cdot \overline{SW1} + \\
 &\overline{SW3} \cdot SW0 + \\
 &\overline{SW1} \cdot SW0 + \\
 &\overline{SW3} \cdot SW2 + \\
 &SW3 \cdot \overline{SW2}
 \end{aligned}$$

A 3
 B 2
 C 1
 D 0

Will be 0 when:

SW3	SW2	SW1	SW0
0	0	1	0
1	1	0	0
1	1	1	0
1	1	1	1

Segment 3

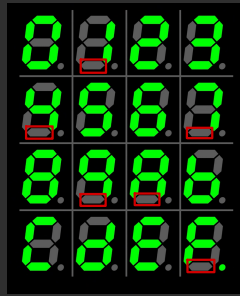

D _{3:0}	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	E
1111	F



	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * SW0$ 1 1	$SW1 * \overline{SW0}$ 1 0
$\overline{SW3} * \overline{SW2}$ 0 0	1	0	1	1
$\overline{SW3} * SW2$ 0 1	0	1	0	1
$SW3 * SW2$ 1 1	1	1	0	1
$SW3 * \overline{SW2}$ 1 0	1	0	1	0


$$\begin{aligned} &\overline{SW3} \cdot \overline{SW2} \cdot \overline{SW0} + \\ &\overline{SW2} \cdot \overline{SW1} \cdot \overline{SW0} + \\ &SW2 \cdot \overline{SW1} \cdot \overline{SW0} + \\ &SW2 \cdot \overline{SW1} \cdot \overline{SW0} + \\ &SW3 \cdot \overline{SW1} \cdot \overline{SW0} \end{aligned}$$

A 3
B 2
C 1
D 0

Will be 0 when:

SW3	SW2	SW1	SW0
0	0	0	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	1	1

Segment 4

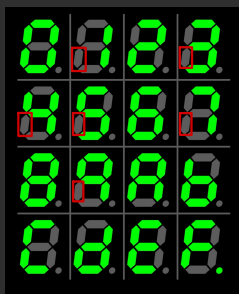

D ₃₋₀	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	E
1111	F



	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * SW0$ 1 1	$SW1 * \overline{SW0}$ 1 0
$\overline{SW3} * \overline{SW2}$ 0 0	1	0	0	1
$\overline{SW3} * SW2$ 0 1	0	0	0	1
$SW3 * SW2$ 1 1	1	1	1	1
$SW3 * \overline{SW2}$ 1 0	1	0	1	1


$$\begin{aligned} \overline{SW2} \cdot \overline{SW0} &+ \\ SW1 \cdot \overline{SW0} &+ \\ SW3 \cdot SW1 &+ \\ SW3 \cdot SW2 & \end{aligned}$$

A 3
B 2
C 1
D 0

Will be 0 when:

SW3	SW2	SW1	SW0
0	0	0	1
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	1
1	0	0	1

Segment 5

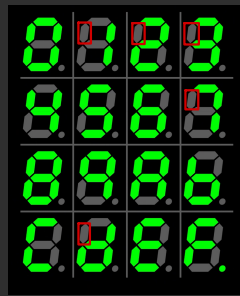

$D_{3:0}$	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	E
1111	F



	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * \overline{SW0}$ 1 1	$SW1 * SW0$ 1 0
$\overline{SW3} * \overline{SW2}$ 0 0	1	0	0	0
$\overline{SW3} * SW2$ 0 1	1	1	0	1
$SW3 * \overline{SW2}$ 1 1	1	0	1	1
$SW3 * SW2$ 1 0	1	1	1	1


$$\begin{aligned}
 &\overline{SW1} \cdot \overline{SW0} + \\
 &SW2 \cdot \overline{SW0} + \\
 &SW3 \cdot \overline{SW2} + \\
 &SW3 \cdot SW1 + \\
 &\overline{SW3} \cdot SW2 \cdot \overline{SW1}
 \end{aligned}$$

A 3
B 2
C 1
D 0

Will be 0 when:

SW3	SW2	SW1	SW0
0	0	0	1
0	0	1	0
0	0	1	1
1	1	0	1

Segment 6

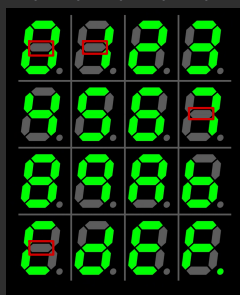

D _{3:0}	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	E
1111	F



	$\overline{SW1} * \overline{SW0}$ 0 0	$\overline{SW1} * SW0$ 0 1	$SW1 * SW0$ 1 1	$SW1 * \overline{SW0}$ 1 0
$\overline{SW3} * \overline{SW2}$ 0 0	0	0	1	1
$\overline{SW3} * SW2$ 0 1	1	1	0	1
$SW3 * \overline{SW2}$ 1 0	0	1	1	1
$SW3 * SW2$ 1 1	1	1	1	1

$$\overline{SW2} \cdot \overline{SW1} +$$

$$SW1 \cdot \overline{SW0} +$$

$$SW3 \cdot \overline{SW2} +$$

$$SW3 \cdot SW0 +$$

$$\overline{SW3} \cdot \overline{SW2} \cdot \overline{SW1}$$

A 3


B 2

C 1




D 0

Will be 0 when:

SW3	SW2	SW1	SW0
0	0	0	1
0	0	1	0
0	0	1	1
1	1	0	1

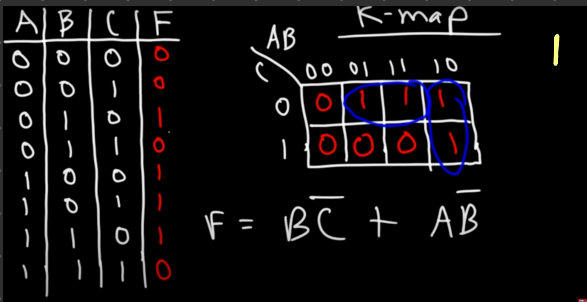

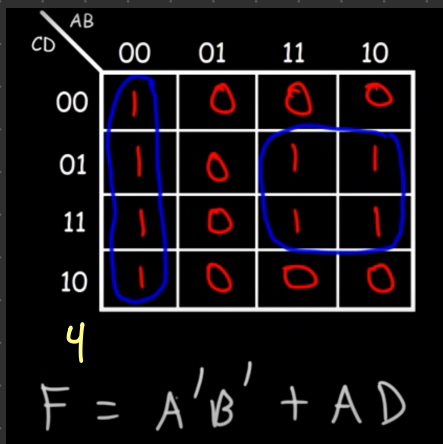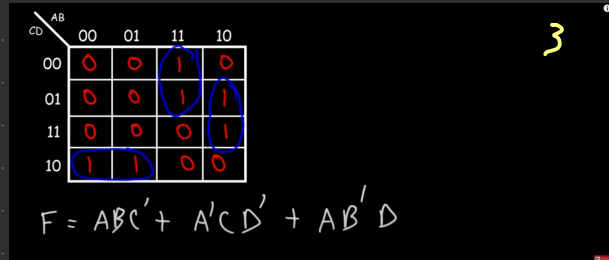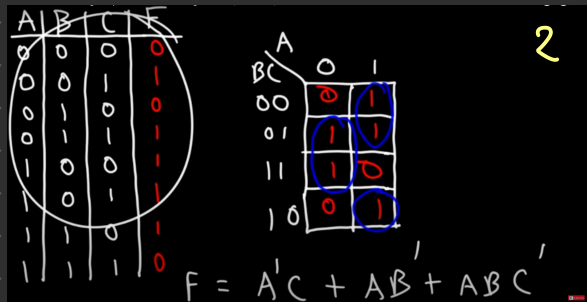- Easier example of k-map grouping
- In 1,2,3 its easy to see the pattern, look at non-changing elements, ignore the rest



- We can apply the same logic for more than 2 boxes

- Note that we can group diagonals

$D_{3:0}$	Character
0000	0
0001	1
0010	2
0011	3
0100	4
0101	5
0110	6
0111	7
1000	8
1001	9
1010	A
1011	b
1100	c
1101	d
1110	e
1111	f

A 3

B 2

C 1

D 0

$$S_0 = (\bar{B} \cdot \bar{D}) + (\bar{A} \cdot C) + (B \cdot C) + (A \cdot \bar{D}) + (\bar{A} \cdot B \cdot D) + (A \cdot \bar{B} \cdot \bar{C})$$

$$S_1 = (\bar{A} \cdot \bar{B}) + (\bar{D} \cdot \bar{B}) + (\bar{D} \cdot \bar{C} \cdot \bar{A}) + (\bar{A} \cdot C \cdot D) + (A \cdot \bar{C} \cdot \bar{D})$$

$$S_2 = (\bar{A} \cdot \bar{C}) + (\bar{A} \cdot D) + (\bar{C} \cdot D) + (\bar{A} \cdot B) + (A \cdot \bar{B})$$

$$S_3 = (\bar{A} \cdot \bar{B} \cdot \bar{D}) + (\bar{B} \cdot C \cdot D) + (B \cdot \bar{C} \cdot D) + (B \cdot C \cdot \bar{D}) + (A \cdot \bar{C} \cdot \bar{D})$$

$$S_4 = (\bar{B} \cdot \bar{D}) + (C \cdot \bar{D}) + (A \cdot C) + (A \cdot B)$$

$$S_5 = (\bar{C} \cdot \bar{D}) + (B \cdot \bar{D}) + (A \cdot \bar{B}) + (A \cdot C) + (\bar{A} \cdot B \cdot \bar{C})$$

$$S_6 = (\bar{B} \cdot C) + (C \cdot \bar{D}) + (A \cdot \bar{B}) + (A \cdot D) + (\bar{A} \cdot B \cdot \bar{C})$$